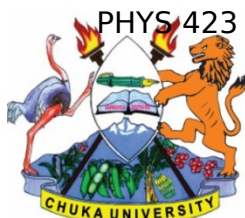


CHUKA



UNIVERSITY

**UNIVERSITY EXAMINATIONS**

**FOURTH YEAR EXAMINATION FOR THE AWARD OF DEGREE OF BACHELOR OF SCIENCE (GENERAL) AND BACHELOR OF EDUCATION (SCIENCE)**

**PHYS 423: ANALOGUE ELECTRONICS**

**STREAMS: B.SC (GENERAL) & B.ED (SC) Y4S2**

**TIME: 2 HOURS**

**DAY/DATE: TUESDAY 09/04/2019**

**11.30 A.M – 1.30 P.M**

**INSTRUCTIONS:**


- Answer question ONE and ANY other TWO questions.

**QUESTION ONE (30 MARKS)**

- (a) Explain why the base of a BJT transistor is lightly doped while the emitter is heavily doped. (2 marks)
- (b) What do you understand by the term “biasing” in transistors (1 mark)
- (c) Differentiate between voltage follower and differential amplifier (2 marks)
- (d) With the help of circuit diagrams, discuss the three basic configurations of the operational Amplifiers (OPAMPS) (3 marks)
- (e) The transistor from a p and n type semiconductor doesn't conduct at 0 V but slight above this value (0.7 V for silicon). Explain this observation (3 marks)
- (f) How is the resistance of a semiconductor material as compared to that of a metal (2 marks)
- (g) Discuss the output transfer characteristics ( $I_C - V_{CE}$ ) of a BJT transistor for various  $V_{BE}$  (4 marks)
- (h) Explain the terms modulation and demodulation as used in electronics (2 marks)
- (i) A transistor amplifier has a gain that varies with frequency. Explain this observation with a curve (Bode plot) (3 marks)
- (j) Class B power amplifiers have zero current when the input signal is zero. With a circuit symbol, explain how it is designed and show its output (5 marks)
- (k) Differentiate between JFET and BJT transistors from their design point of view (3 marks)

**QUESTION TWO (20 MARKS)**

- (a) Figure 2.1 shows an operational amplifier circuit that was used in the input stage of a loudspeaker. The source voltage ( $V_{in}$ ) is sinusoidal and there are no distortion of the output voltage ( $V_{out}$ ).

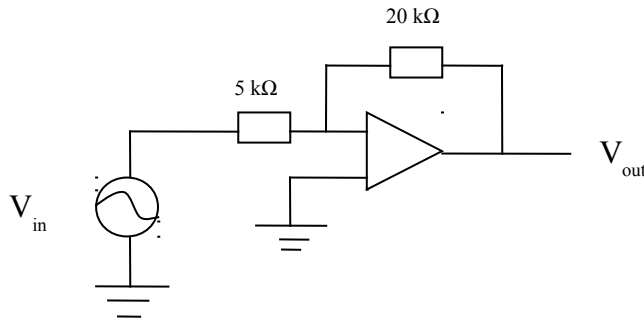

**Figure 2.1.** Operational amplifier circuit

- (i) Sketch the waveform for the output voltage in relation to that of the input voltage.  
Explain your answer. (3 marks)
- (ii) Calculate the voltage gain of this amplifier configuration (3 marks)
- (b) Class B push pull amplifiers are known to have cross over distortion problems. With the help of a waveform, discuss the effect of this problem in sound producing devices ie loudspeaker (6 marks)
- (c) With a well labeled circuit diagram, show the circuit symbol of n-channel and p-channel MOSFET (4 marks)
- (d) For high amplification, a multistage transistor amplifier is preferred. Describe how this is designed (4 marks)

**QUESTION THREE (20 MARKS)**

- (a) With circuit diagrams, describe how an operational amplifier is configured as an integrator and a differentiator (6 marks)

- (b) Figure 3.1 shows a two stage current amplifier used in a sensor circuit with BJT transistors  $Tr_1$  and  $Tr_2$ .

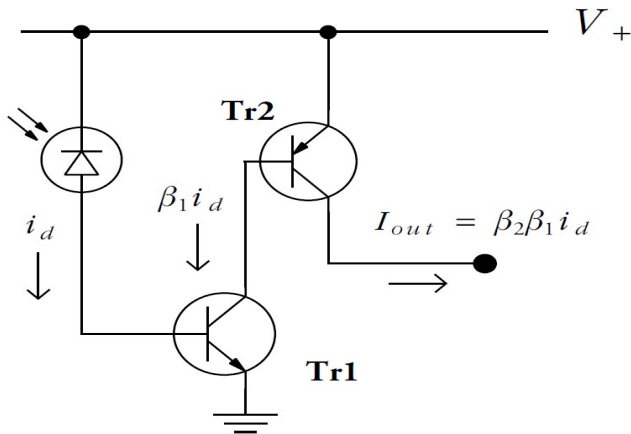


Figure 3.1. A two stage current amplifier based on BJT transistors.

- (i) Briefly explain how the current  $i_d$  is generated in the circuit when light falls on the given diode as shown. (3 marks)
- (ii) What is the purpose of  $V_+$  voltage connected to the transistor  $Tr_2$  and the diode (2 marks)
- (iii) Given  $\beta_1 = 200$  and  $\beta_2 = 100$ , calculate the gain of the two stage current amplifier (4 marks)
- (iv) Describe one practical application of the above circuit in security surveillance with slight addition of electronics components if any (3 marks)
- (c) An OPAMP can be applied as a summing amplifier. Describe how this is designed (2 marks)

**QUESTION FOUR (20 MARKS)**

- (a) An n-p-n transistor circuit is given in figure 4.1 with  $\beta = 100$  and the transistor is made of silicon ie  $V_{BE} = 0.7 V$ .

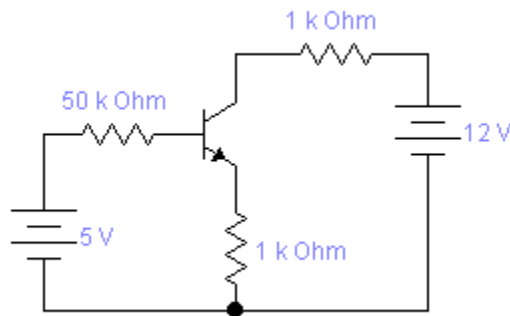


Figure 4.1. n-p-n transistor circuit.

Compute the following parameters for the given transistor


- (i)  $I_B$  (4 marks)
- (ii)  $I_C$  (2 marks)

- (iii)  $I_E$  (2 marks)
- (iv)  $V_{CE}$  (3 marks)

- (b) With a well labeled diagram, describe how the following diodes operate: Shotky diode, Zener diode and tunnel diode (6 marks)
- (c) Explain why intrinsic semiconductor doesn't conduct electricity at room temperature (3 marks)

**QUESTION FIVE (20 MARKS)**

- (a) Figure 5.1 shows a bipolar junction transistor amplifier circuit that was used in the input stage of a sensor. If the source voltage ( $V_{in}$ ) is equal to  $V_B$ , show that, the voltage gain of this amplifier is given by  $-R_C/R_E$ . (8 marks)

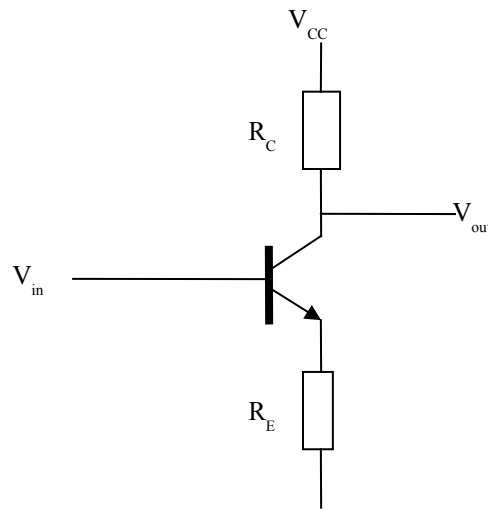

**Figure 5.1.** BJT amplifier circuit

- (b) With a well labeled diagram, describe how a junction field effect transistor with n-channel is constructed (6 marks)
  - (c) Discuss the input characteristics ( $I_B - V_{BE}$ ) of a BJT transistor for various  $V_{CE}$  (4 marks)
  - (d) An OPAMP can be applied as a integrator amplifier. Describe how this is designed (2 marks)
-